

Register file construction

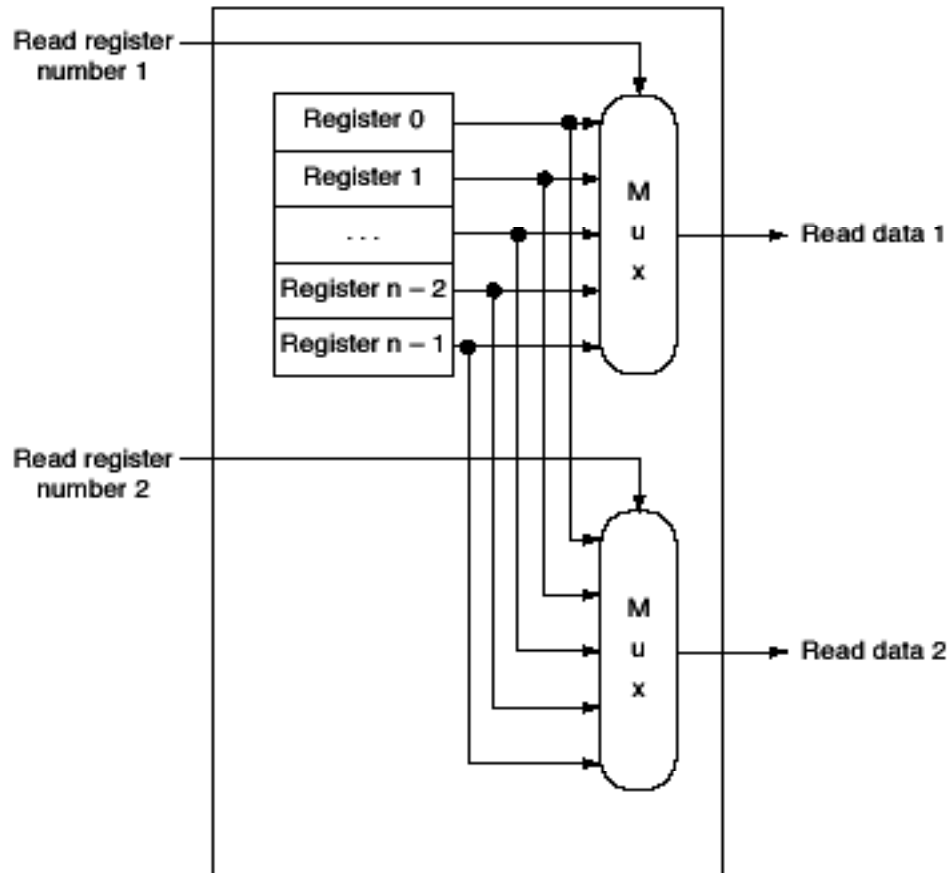


FIGURE B.8.8 The implementation of two read ports for a register file with n registers can be done with a pair of n -to-1 multiplexers each 32 bits wide. The register read number signal is used as the multiplexer selector signal. Figure B.8.9 shows how the write port is implemented.

Creating read ports


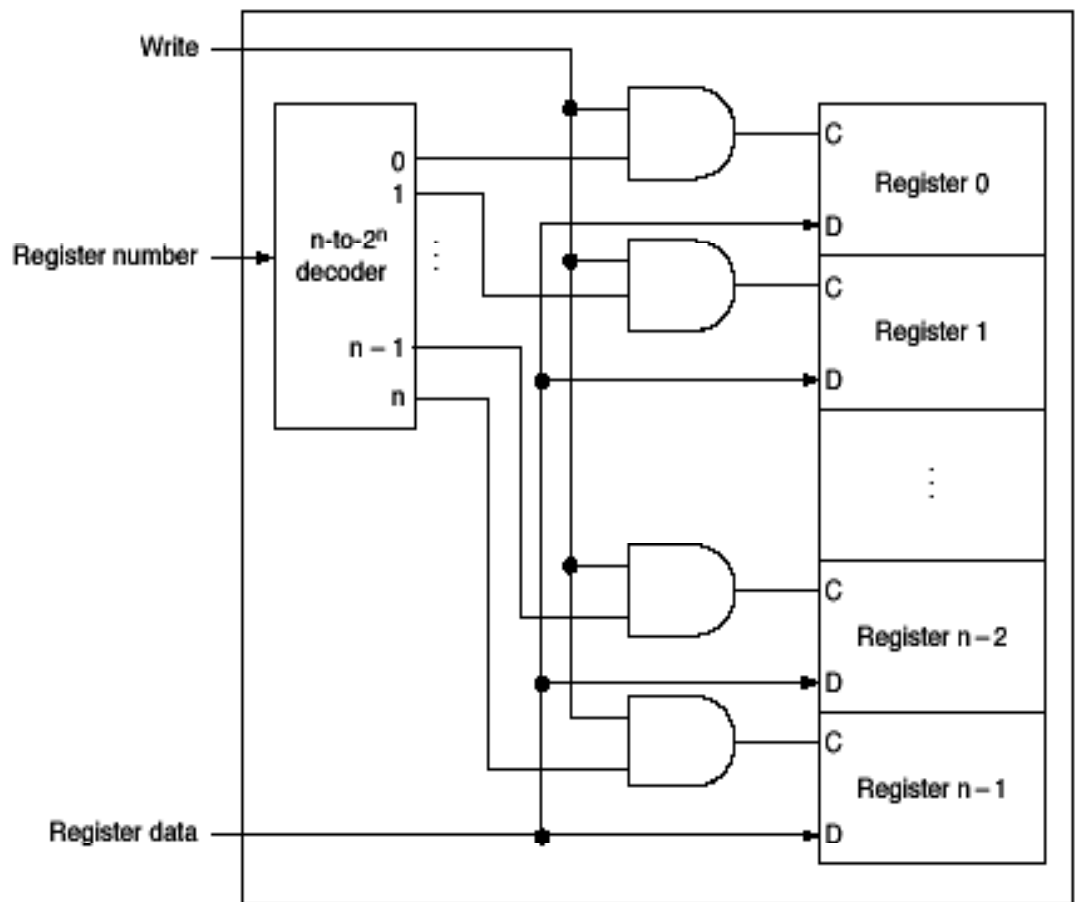
 


FIGURE B.8.9 The write port for a register file is implemented with a decoder that is used with the write signal to generate the *C* input to the registers. All three inputs (the register number, the data, and the write signal) will have set-up and hold-time constraints that ensure that the correct data is written into the register file.


Creating write port

Main Memory

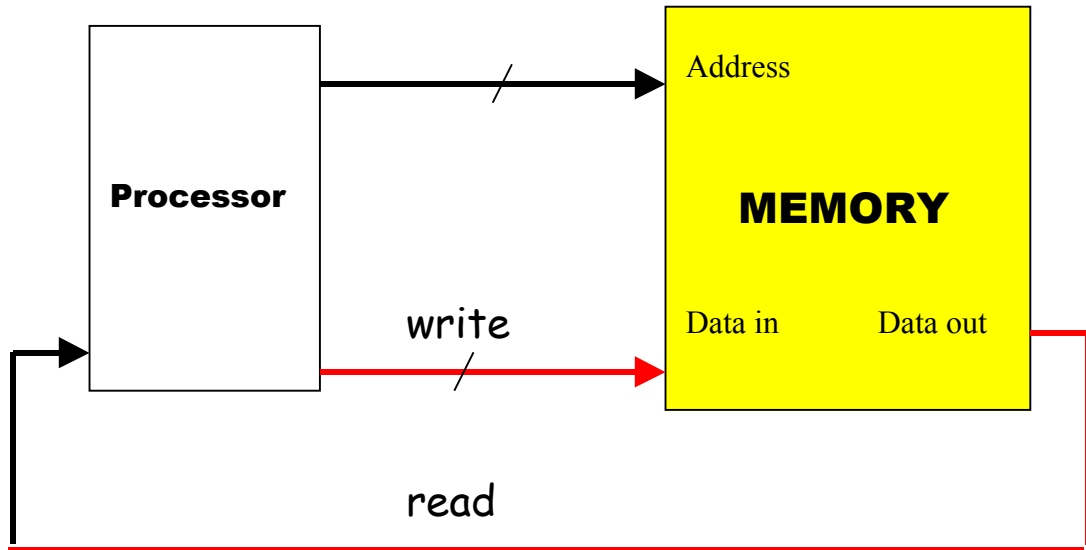

Typical sizes of SRAM are

 (32 or 64 or 128 or 256) × (1 or 2 or 4 or 8 bits)



How many lines are there in **address**, **data in** and **data out**?


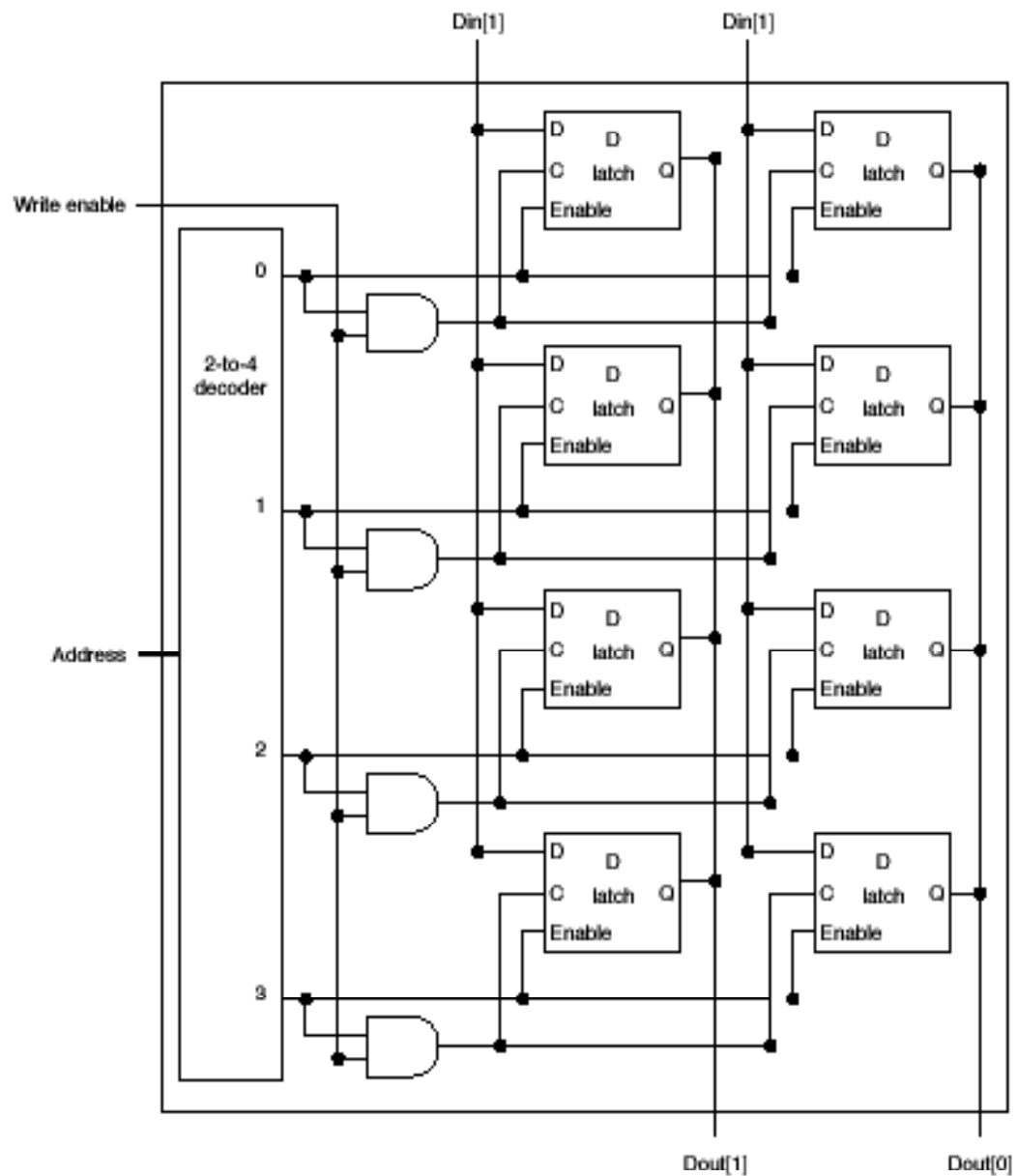



FIGURE B.9.3 The basic structure of a 4×2 SRAM consists of a decoder that selects which pair of cells to activate. The activated cells use a three-state output connected to the vertical bit lines that supply the requested data. The address that selects the cell is sent on one of a set of horizontal address lines, called the word lines. For simplicity, the Output enable and Chip select signals have been omitted, but they could easily be added with a few AND gates.

32K x 1 bit RAM using 4 8K x 1 RAMs

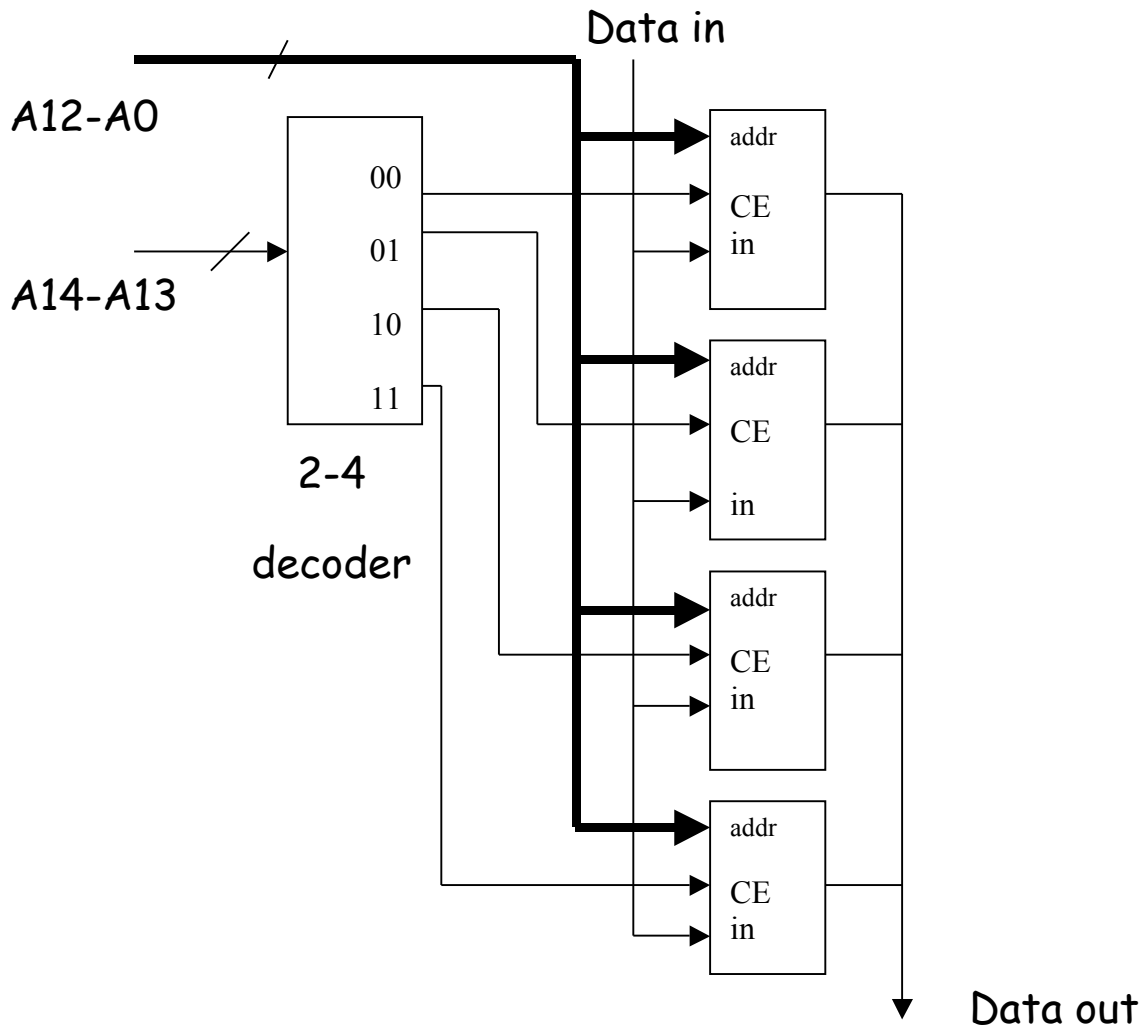

For each chip, the write enable line is set to 1 during a write operation, and the output enable lines are set to 1 during a read operation.

32Kx 4 bit RAM using 32K x 1 bit RAMs

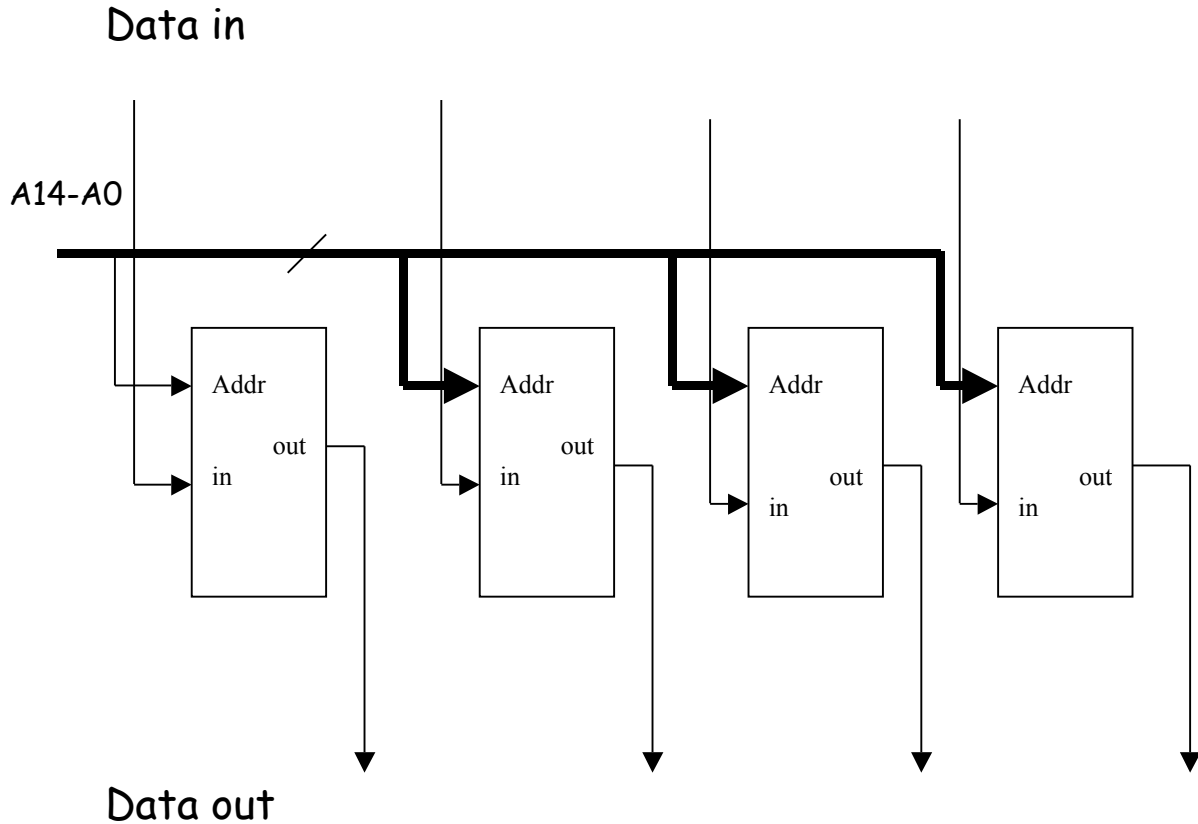

For each chip, the write enable line is set to 1 during a write operation, and the output enable lines are set to 1 during a read operation.