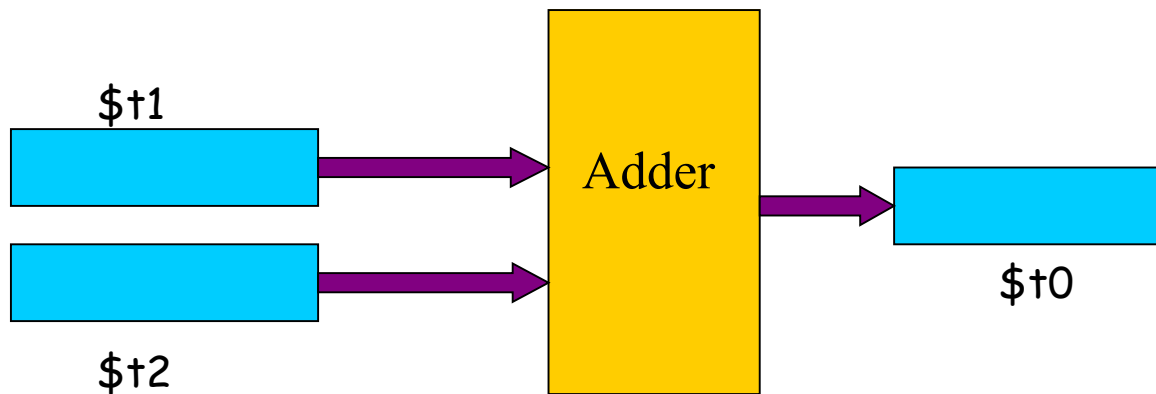


Understanding Logic Design

(Appendix C of your Textbook on the CD)

When you write `add $t0, $t1, $t2`, you imagine something like this:




What kind of hardware can ADD two binary integers?

We need to learn about *GATES* and *BOOLEAN ALGEBRA* that are foundations of logic design.


AND gate

X	Y	X.Y
0	0	0
0	1	0
1	0	0
1	1	1

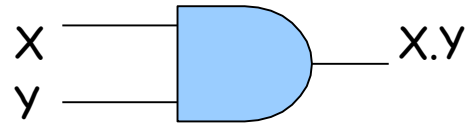


OR gate

X	Y	X+Y
0	0	0
0	1	1
1	0	1
1	1	1

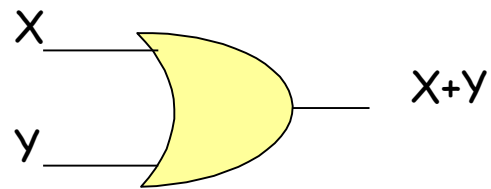


NOT gate

X	\overline{X}
0	1
1	0

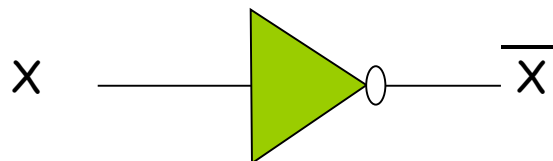

Typically, logical 1 = +3.5 volt, and logical 0 = 0 volt. Other representations are possible.

Analysis of logical circuits

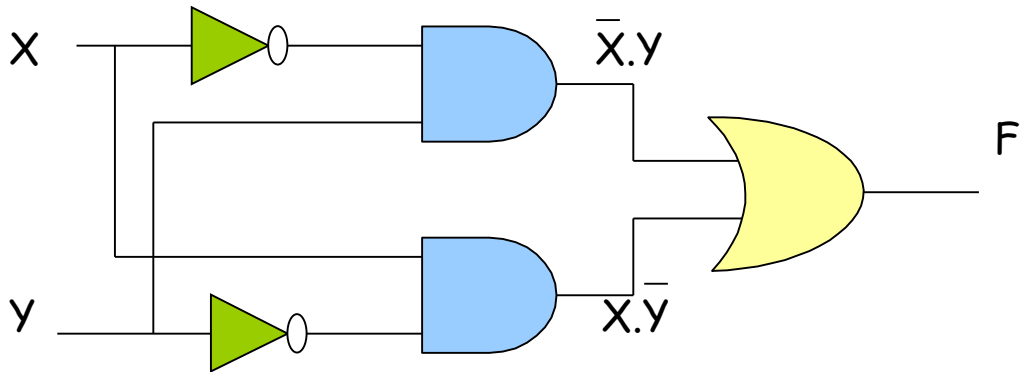

What is the value of F when X=0 and Y=1?

Draw a truth table.

X	Y	F
0	1	0
0	1	1
1	0	1
1	1	0

This is the **exclusive or** (XOR) function. In algebraic


form $F = \bar{X}.Y + X.\bar{Y}$

More practice

1. Let $\bar{A}.B + A.C = 0$. What are the values of A, B, C ?

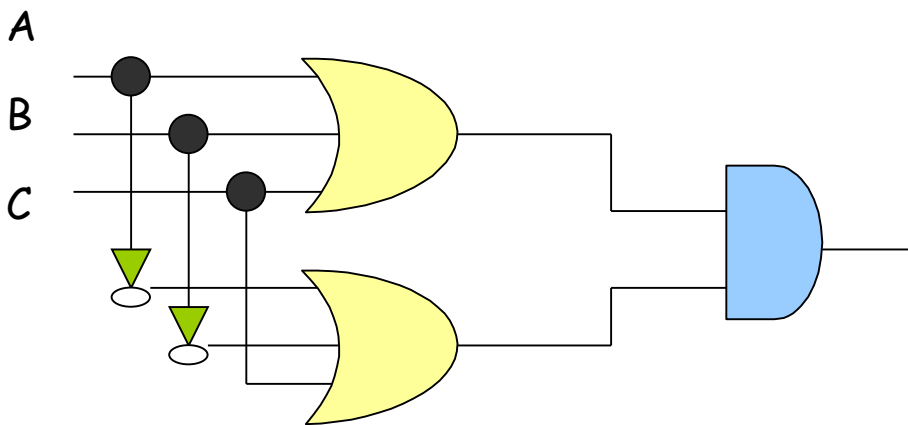1. Let $(A + B + C).(A + B + C) = 0$. What are the possible values of A, B, C ?

- Draw truth tables.
- Draw the logic circuits for the above two functions.



Elementary Boolean Algebra

$$\left. \begin{array}{l} A + 0 = A \\ A \cdot 1 = A \end{array} \right\}$$

$$A + A' = 1$$

$$A \cdot A' = 0$$

$$\left. \begin{array}{l} 1 + A = 1 \\ 0 \cdot A = 0 \end{array} \right\}$$

$$\left. \begin{array}{l} A + B = B + A \\ A \cdot B = B \cdot A \end{array} \right\}$$

$$\left. \begin{array}{l} 0 + A = A \\ 0 + A = A \end{array} \right\}$$

$$\left. \begin{array}{l} A + (B + C) = (A + B) + C \\ A \cdot (B \cdot C) = (A \cdot B) \cdot C \end{array} \right\}$$

$$\left. \begin{array}{l} A + A = A \\ A \cdot A = A \end{array} \right\}$$

$$\left. \begin{array}{l} A \cdot (B + C) = A \cdot B + A \cdot C \\ A + B \cdot C = (A + B) \cdot (A + C) \end{array} \right\} \text{Distributive Law}$$

$$\left. \begin{array}{l} \overline{A \cdot B} = \overline{A} + \overline{B} \\ \overline{A + B} = \overline{A} \cdot \overline{B} \end{array} \right\} \text{De Morgan's theorem}$$